

भारतीय प्रौद्योगिकी संस्थान धारवाड़ Indian Institute of Technology Dharwad

# Reconfigurable Rectifier for RF Energy Harvesting System at WiFi-6 Frequency Band for 2.5 V

Authors: Mouli Venkata Prakash, Aditya Kalyani, Nagaveni S




#### Content

- Introduction.
- Block diagram of RF Energy Harvesting
- Problem Statement
- Significance Of Reconfigurable Rectifier.
- Proposed RF Energy Harvester With Reconfigurable Rectifier.
  - Matching Network
  - Reconfigurable Rectifier and its working.
  - Low Drop-out Regulator
- Simulation Result.
- Conclusion.



What is Energy Harvesting

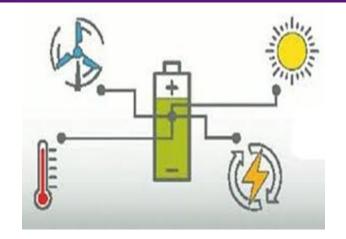Conversion of ambient energy into electrical Energy



Need of Energy Harvesting

- To extend the Battery life
- Self power




Why RF?


- Ubiquitous
- Easy to introduce in Wireless sensor nodes


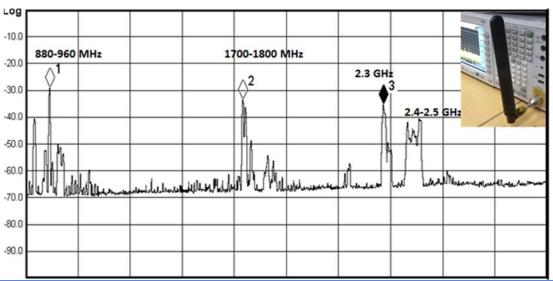
## **Survey of Ambient RF Power**

• Received RF power using immobile R&S FSW50 spectrum analyser and a wideband antenna with a gain of 5 dBi.



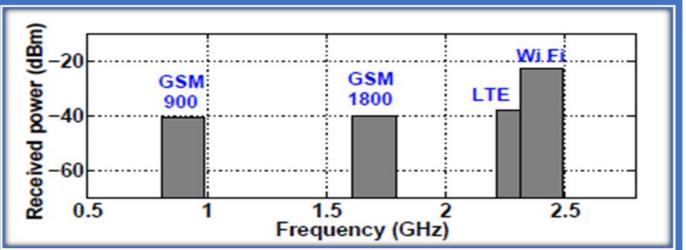

#### State-of-the-art challenges


- Scavenging lower input power levels
- RF power is spread across multiple
  bands
- Variation in input power levels
- Antenna to rectifier matching
- Minimization of controller power consumption

#### Content

- Introduction.
- Block diagram of RF Energy Harvesting
- Problem Statement
- Significance Of Reconfigurable Rectifier.
- Proposed RF Energy Harvester With Reconfigurable Rectifier.
  - Matching Network
  - Reconfigurable Rectifier and its working.
  - Low Drop-out Regulator
- Simulation Result.
- Conclusion.



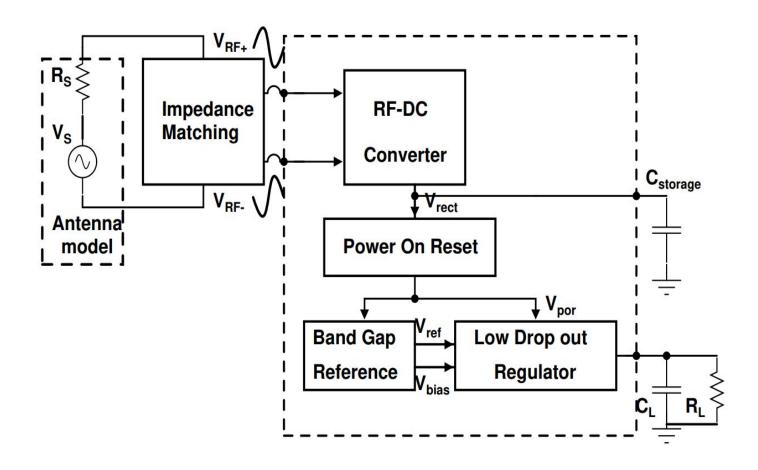
## **Block Diagram of RF Energy Harvesting**



#### **Problem Statement:**

- Fluctuations in input power, influenced by time and distance, introduce changes in the rectifier's impedance and disrupt its optimized operational conditions.
- Rectifier stages need to be configured for effective operation across a wide range of input power levels.

### **Problem Statement:**

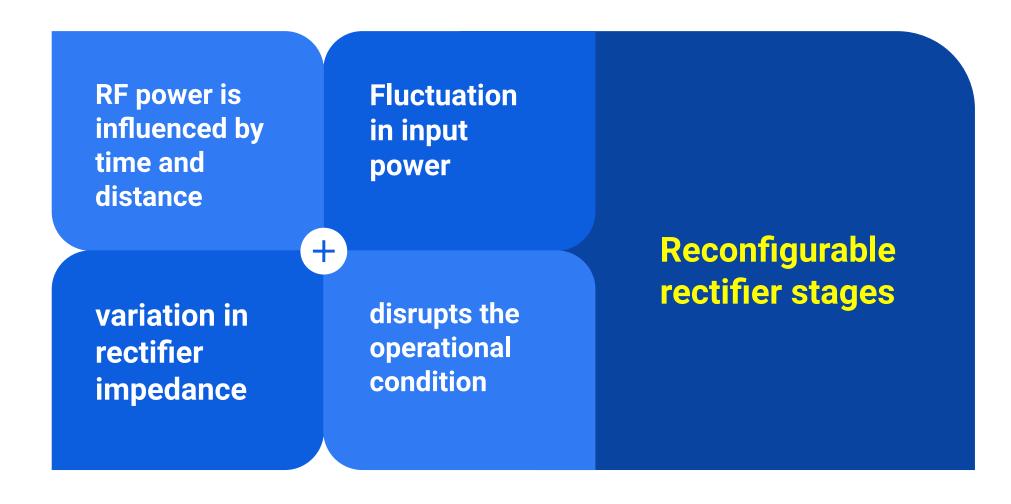


#### Content

- Introduction.
- Block diagram of RF Energy Harvesting
- Problem Statement
- Significance Of Reconfigurable Rectifier
- Proposed RF Energy Harvester With Reconfigurable Rectifier.
  - Matching Network
  - Reconfigurable Rectifier and its working.
  - Low Drop-out Regulator
- Simulation Result.
- Conclusion.



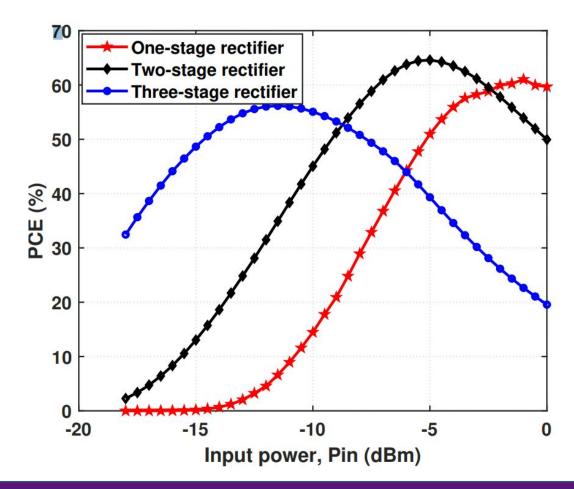
## 1. PCE of rectifier stages with respect to input power

- Degradation observed at lower and higher power levels due to impedance mismatch.
- Single-stage rectifier recommended at -14 dBm for efficient power conversion.
- Two-stage rectifier performs best at -5 dBm, ensuring optimal power conversion efficiency.



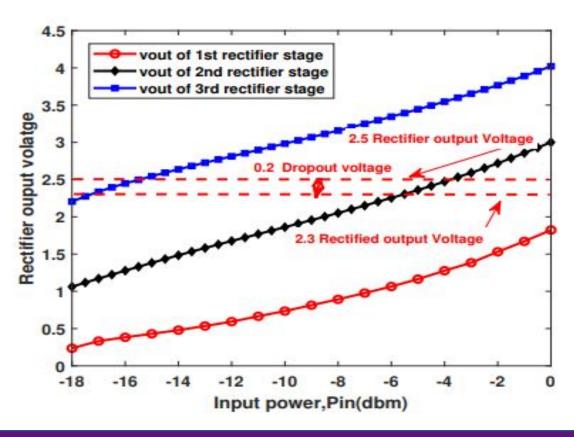
## 2. Input Power vs. Rectifier Stages


- Lower input power requires more rectifier stages.
- Higher input power requires fewer rectifier stages.


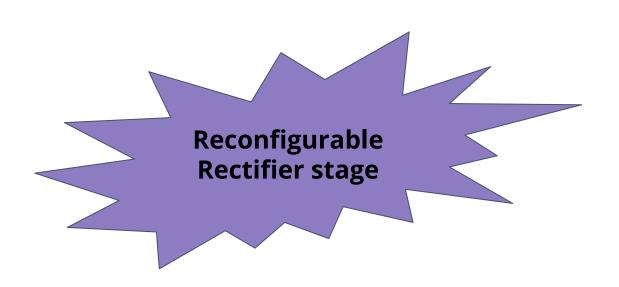
## 3. Input Voltage vs. LDO Efficiency:

- Optimal efficiency is achieved by setting the input voltage to the regulated voltage plus the dropout voltage.
- Maintaining the input voltage within this range enhances LDO efficiency and overall performance.



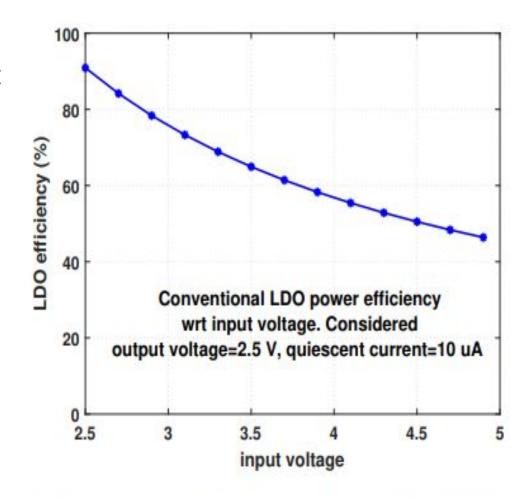


#### **Content**

- Introduction.
- Block diagram of RF Energy Harvesting
- Problem Statement
- Significance Of Reconfigurable Rectifier
- Proposed RF Energy Harvester With Reconfigurable Rectifier
  - Matching Network
  - Reconfigurable Rectifier and its working.
  - Low Drop-out Regulator
- Simulation Result.
- Conclusion.



## **Reconfigurable Rectifier:**

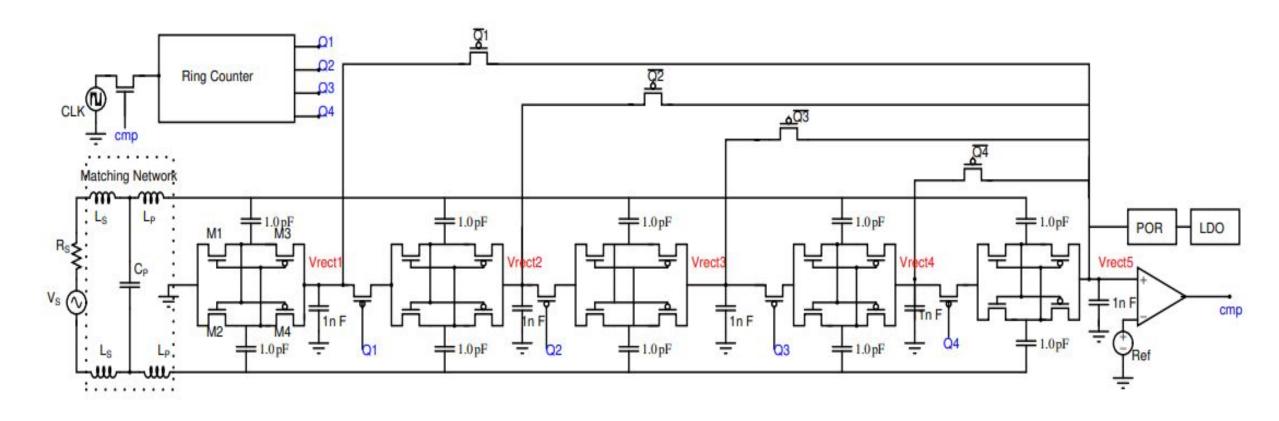

Block diagram (Rectifier: M1 = M2 = 3.6  $\mu$ m / 0.18  $\mu$ m, M3 = M4 = 18  $\mu$ m / 0.18  $\mu$ m)


## **Matching Network:**


- Impedance matching ensures efficient power transfer from RF source to the load.
- Low to high matching impedance is given as

$$Z_0 = jX_{Ls} + (R_i||-jX_{c_{pleft}})$$


High to Low matching impedance is given as

$$R_i = (jX_{Lp} + R_L)||-jX_{c_{pright}}|$$

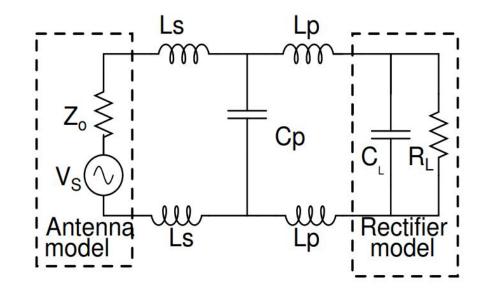

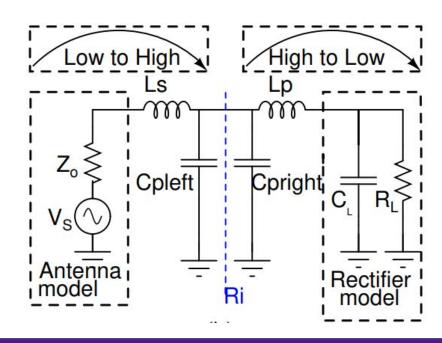


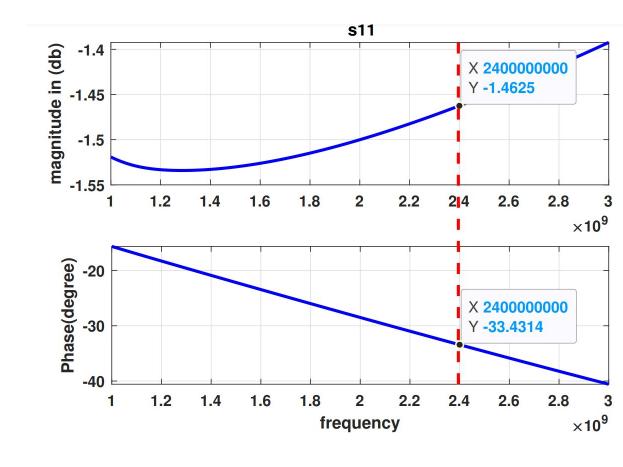- Impedance of the rectifier is determined using Large Signal Small-Signal Power (LSSP) analysis and Harmonic Balance (HB) analysis in Cadence Virtuoso
- The magnitude and phase of ZL at 2.4 GHz without impedance matching is -1.465 dB and -33.43 degrees at 2.4 GHz.
- Ls ,Lp and CP values can be found using Ri and ZL values.




- $S11 = 10^{(-18/10)} = 0.0158$ .
- Pin = Ps(1 |S11|) which makes efficiency

$$P_{in}/P_{s}=94.37\%$$
.

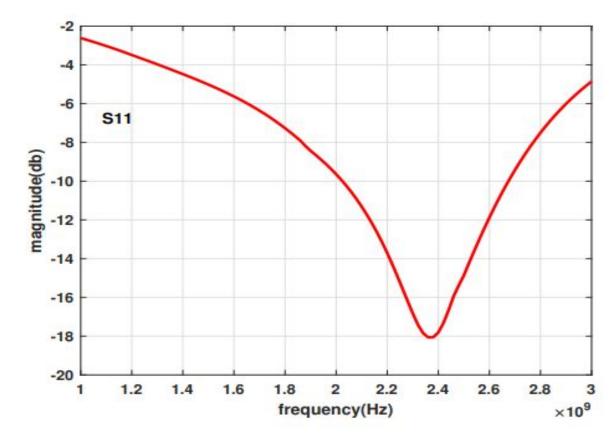


**S11 PLot with impedance matching** 

## Working of Reconfigurable Rectifier:

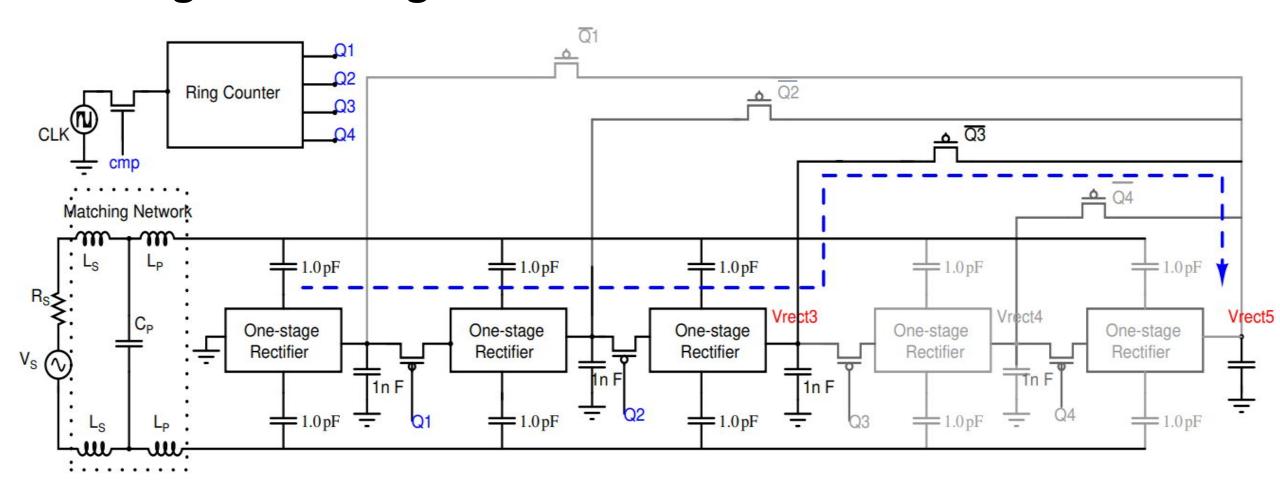


Circuit behaviour as three-stage rectifier at Ps = -5 dBm

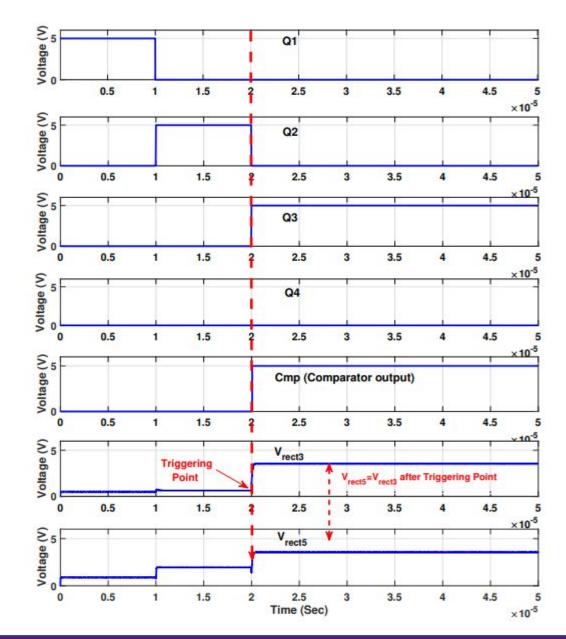- Q3 high state turns off its MOSFET, blocking power to the next stage.
- Q3 MOSFET also shorts third stage output to the final stage.
- Q1 and Q2 switches enable power flow to the third stage.
- Third stage output above 2.5 V triggers the comparator, producing a high output which halts the ring counter.



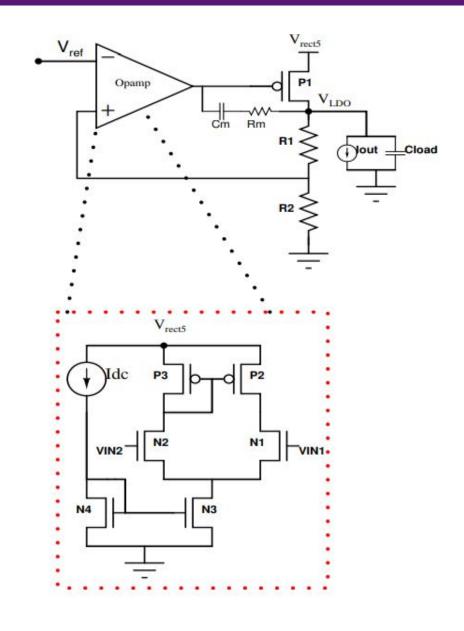
## LDO (Low Dropout Regulator):

- The LDO schematic integrates NMOS and PMOS transistors.
- The specific compensating components are a 600 fF Miller capacitor and a 1.6 kOhm resistor.
- These components aim to achieve the desired phase margin and bandwidth.
- Resistors R1 and R2 are tailored to attain a 2.3 V output with a 1.725 V reference signal.



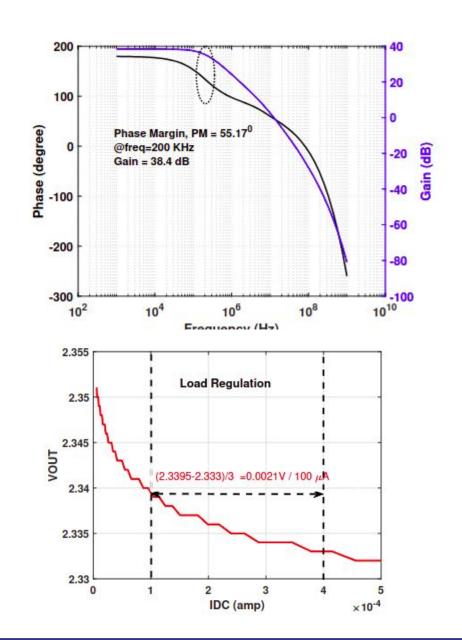
#### **LDO**

- The reconfigurable rectifier is followed up with a LDO to showcase the performance of the system.
- The LDO clearly depicts the stability of the system with a phase margin greater than 57 degree, along with a dc gain of greater then 38 dB.
- A load regulation of 2.1 mV for 100 μA change of current and a line variation of 5mV for 1V change of input line voltage is seen.


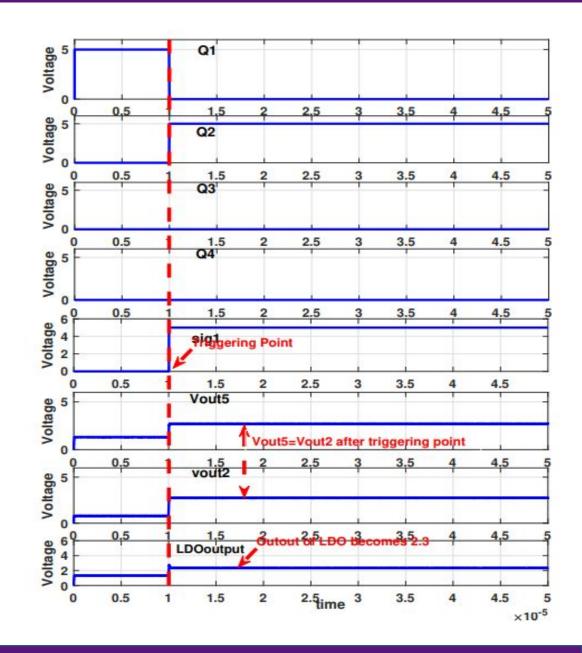
#### **SIMULATION RESULTS:**

- When Q2 is high, it deactivates the corresponding MOSFET Q2.
- Deactivation of Q2 prevents power flow to the next stage.
- It effectively shorts the output of the second rectifier stage to the final rectifier stage.
- Q1 switch facilitates power flow to the second stage.



- Since Power connection is maintained until there's a change in input power the Rectifier output voltage is maintained above 2.5 V, which subsequently directed to an LDO circuit.
- The LDO circuit ensures a stable, regulated output voltage of 2.3 V.
- This stability is maintained even with fluctuating input voltage.

#### **CONCLUSION**

- The proposed system facilitates reconfiguration to the relevant stage, ensuring maintenance of the desired voltage level while optimizing efficiency.
- Impedance-matching network values were determined through a large signal SP analysis to derive the rectifier's impedance.
- The system achieves a sensitivity of -14 dBm.
- The rectifier output voltage is stabilized at 2.5 V, with a regulated output of 2.3 V.

# **Thank You**