



॥ सा विद्या या विमुक्तये ॥

भारतीय प्रौद्योगिकी संस्थान धारवाड़

Indian Institute of Technology Dharwad

# CALIBRATING CIRCUITS FOR RF ENERGY HARVESTING

MOULI VENKATA PRAKASH PITTALA


GUIDED BY: PROF S NAGAVENI

# ABSTRACT


- To Demonstrate an Impedance matching network and reconfigurable rectifier stages in RF energy harvesting system, to be used with a passive wearable device operating at a distance of 6-20 m from a wireless power source.
- This RF energy harvesting circuit can harvest an input power as low as -14 dBm from both 925 MHz and 2.4 GHz, ISM frequencies.
- Circuit is implemented in a standard 0.18  $\mu\text{m}$  CMOS technology.
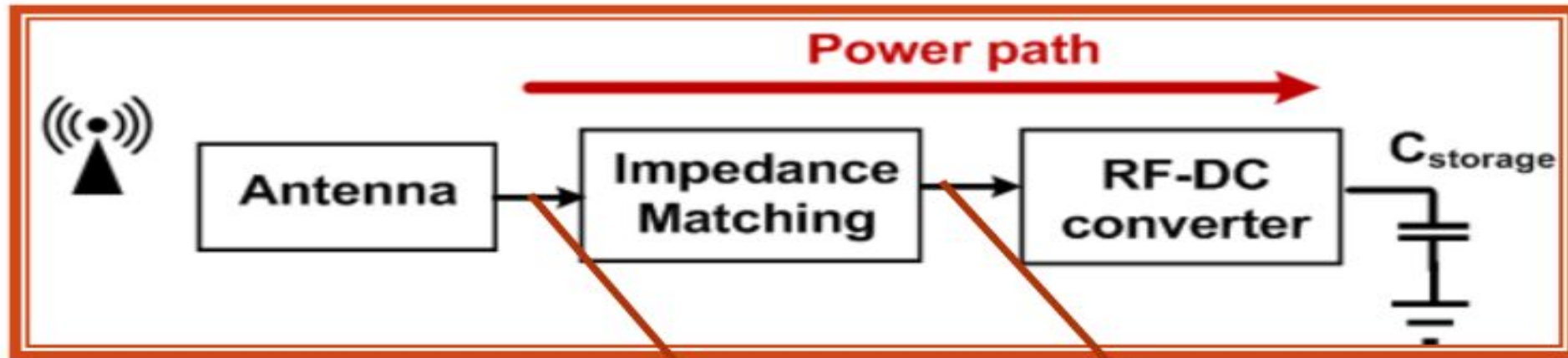
# Motivation

- The received RF input power varies with time and distance.
- These variations in the input power causes the change in the impedance of the rectifier.
- Hence an impedance calibration circuit is required to tune the matching network values .
- Low powered signal needed to be multiplied through multiple stages of rectification.so an reconfiguration circuit for number of stages is required.



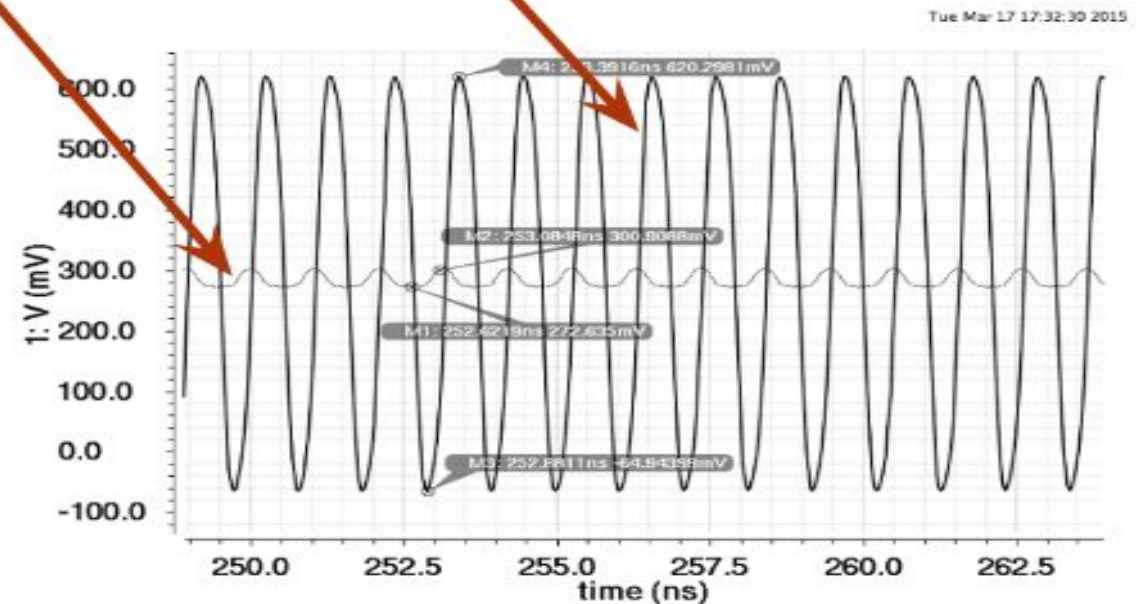- Antenna – To receive RF power
- Impedance matching network- For maximum power transfer and passive voltage boosting
- RF-DC converter (Rectifier) – To convert AC signal; to DC



# ANTENNA

- If  $P_{avail}$  is the power available at the input terminals of a receiving antenna and  $R_a$  is the radiation resistance of the antenna then the open circuited voltage ( $V_a$ ) developed across the antenna terminals can be found from the following equation.

$$P_{avail} = \frac{V_a^2}{8R_a}$$

# Impedance Matching Calibration network

# IMPEDANCE MATCHING NETWORK

- An impedance matching network (MN) between the antenna and rest of the circuitry in any RF system helps in transferring the maximum available power from the output of the antenna to the rest of the circuitry.
- Components used in IMN
  - Thermal counter
  - capacitors
  - Inductors(LC Circuit)

```

module first_counter (clock , reset , enable ,counter_out );
input clock ;
input reset ;
input enable ;
output [3:0] counter_out ;
wire clock ;
wire reset ;
wire enable ;
reg [3:0] counter_out ;
reg [3:0] a;
always @ (posedge clock)
begin : COUNTER
    if (reset == 1'b1) begin
        counter_out <= 4'b0001;
    end
    else if (enable == 1'b1) begin
        counter_out <= counter_out | (counter_out<<1) ;
    end
end
endmodule
module first_counter_tb();
reg clock, reset, enable;
wire [3:0] counter_out;
initial begin
    $display ("time\t clk reset enable counter");
    $monitor ("%g\t %b %b %b %b",$time, clock, reset, enable, counter_out);
    clock = 1;          // initial value of clock
    reset = 0;          // initial value of reset
    enable = 0;         // initial value of enable
    #1 reset = 1;       // Assert the reset
    #2 reset = 0;       // De-assert the reset
    #1 enable = 1;      // Assert enable
    #5 enable = 0;      // De-assert enable
    $finish;           // Terminate simulation
end

// Clock generator
always begin
    #1 clock = ~clock; // Toggle clock every 5 ticks
end
first_counter mouli (clock,reset,enable,counter_out);
endmodule

```

## VERILOG CODE OF THERMAL COUNTER



```

module first_counter (clock , reset , enable ,counter_out );
input clock ;
input reset ;
input enable ;
output [3:0] counter_out ;
wire clock ;
wire reset ;
wire enable ;
reg [3:0] counter_out ;
reg [3:0] a;
always @ (posedge clock)
begin : COUNTER
    if (reset == 1'b1) begin
        counter_out <= 4'b0000;
    end
    else if (enable == 1'b1) begin
        counter_out <= counter_out +1 ;
    end
end
end
endmodule
module first_counter_tb();
reg clock, reset, enable;
wire [3:0] counter_out;
initial begin
    $display ("time\t clk reset enable counter");
    $monitor ("%g\t %b %b %b %b", $time, clock, reset, enable, counter_out);
    clock = 1; // initial value of clock
    reset = 0; // initial value of reset
    enable = 0; // initial value of enable
    #1 reset = 1; // Assert the reset
    #2 reset = 0; // De-assert the reset
    #1 enable = 1; // Assert enable
    #29 enable = 0; // De-assert enable
    $finish; // Terminate simulation
end

// Clock generator
always begin
    #1 clock = ~clock; // Toggle clock every 5 ticks
end
first_counter mouli (clock,reset,enable,counter_out);
endmodule

```


## VERILOG CODE OF BINARY COUNTER


```

mouli@mouli-Victus-by-HP-Laptop-16-e0xxx:~/Desktop/m_v$ iverilog thermalcounter.v
mouli@mouli-Victus-by-HP-Laptop-16-e0xxx:~/Desktop/m_v$ vvp a.out
time    clk reset enable counter
0       1  0    0      xxxx
1       0  1    0      xxxx
2       1  1    0      0001
3       0  0    0      0001
4       1  0    1      0011
5       0  0    1      0011
6       1  0    1      0111
7       0  0    1      0111
8       1  0    1      1111
9       0  0    0      1111
mouli@mouli-Victus-by-HP-Laptop-16-e0xxx:~/Desktop/m_v$ iverilog binarycounter.v
mouli@mouli-Victus-by-HP-Laptop-16-e0xxx:~/Desktop/m_v$ vvp a.out
time    clk reset enable counter
0       1  0    0      xxxx
1       0  1    0      xxxx
2       1  1    0      0000
3       0  0    0      0000
4       1  0    1      0001
5       0  0    1      0001
6       1  0    1      0010
7       0  0    1      0010
8       1  0    1      0011
9       0  0    1      0011
10      1  0    1      0100
11      0  0    1      0100
12      1  0    1      0101
13      0  0    1      0101
14      1  0    1      0110
15      0  0    1      0110
16      1  0    1      0111
17      0  0    1      0111
18      1  0    1      1000
19      0  0    1      1000
20      1  0    1      1001
21      0  0    1      1001
22      1  0    1      1010
23      0  0    1      1010
24      1  0    1      1011
25      0  0    1      1011
26      1  0    1      1100
27      0  0    1      1100
28      1  0    1      1101
29      0  0    1      1101
30      1  0    1      1110
31      0  0    1      1110
32      1  0    1      1111
33      0  0    0      1111
mouli@mouli-Victus-by-HP-Laptop-16-e0xxx:~/Desktop/m_v$


```


## Output of Thermal and binary counter

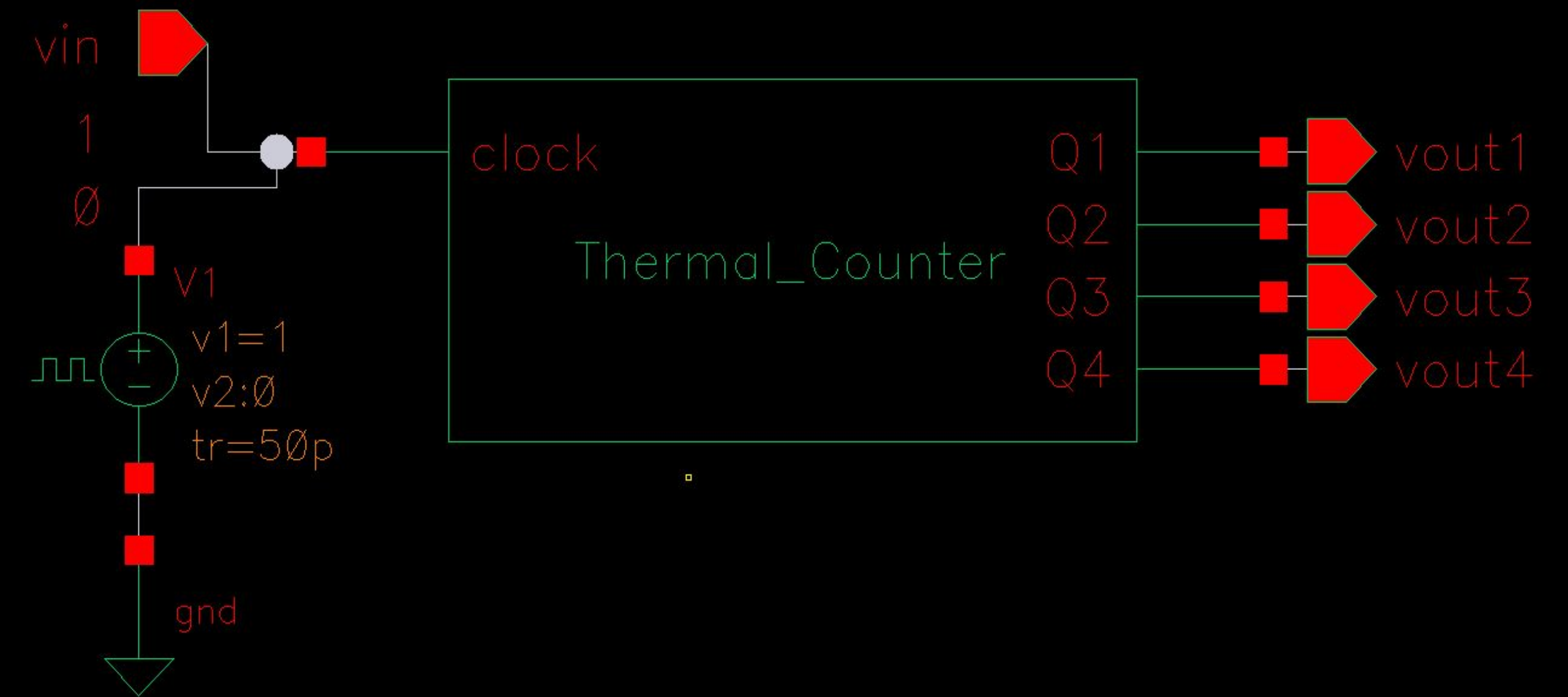


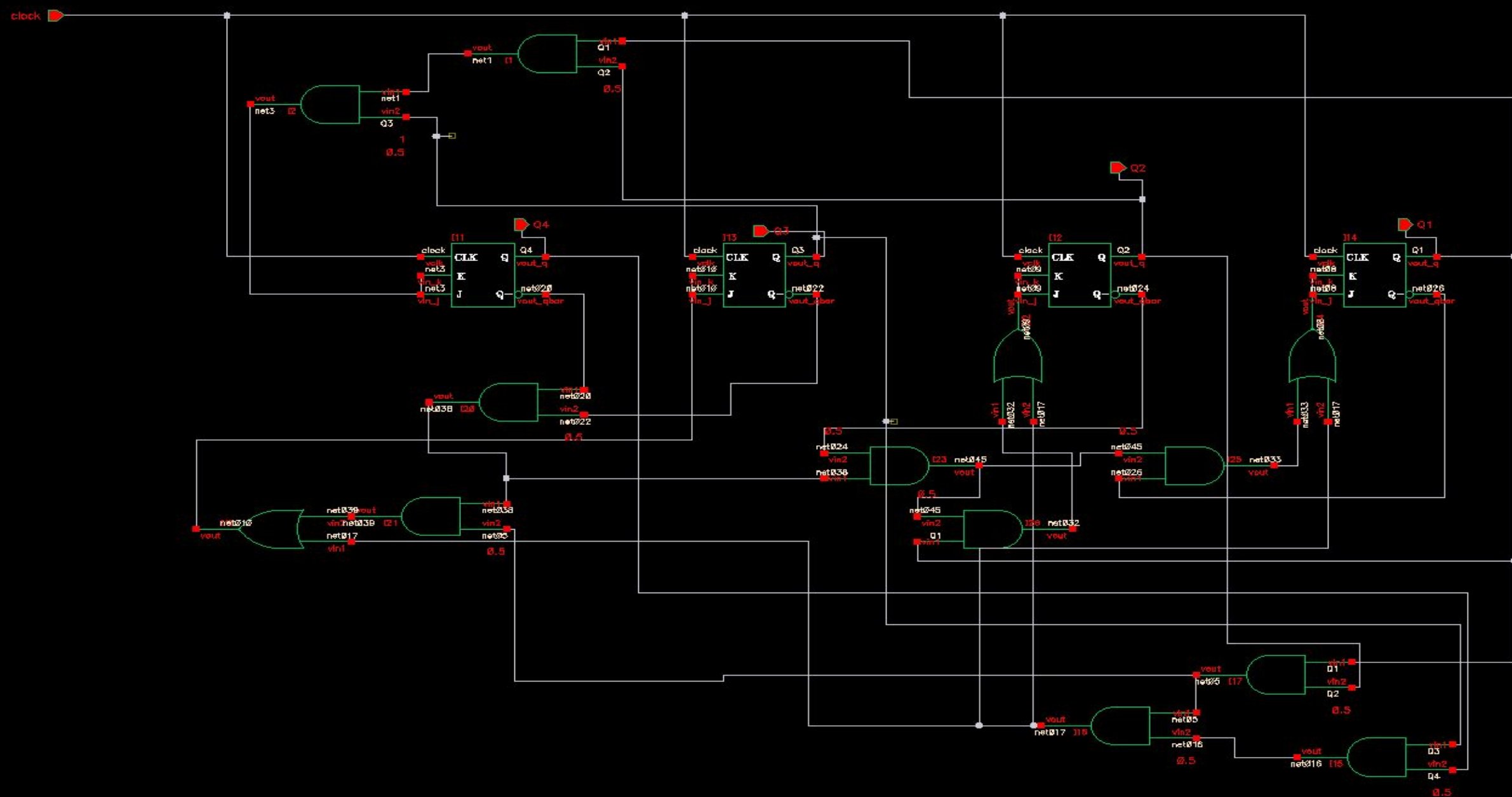



 

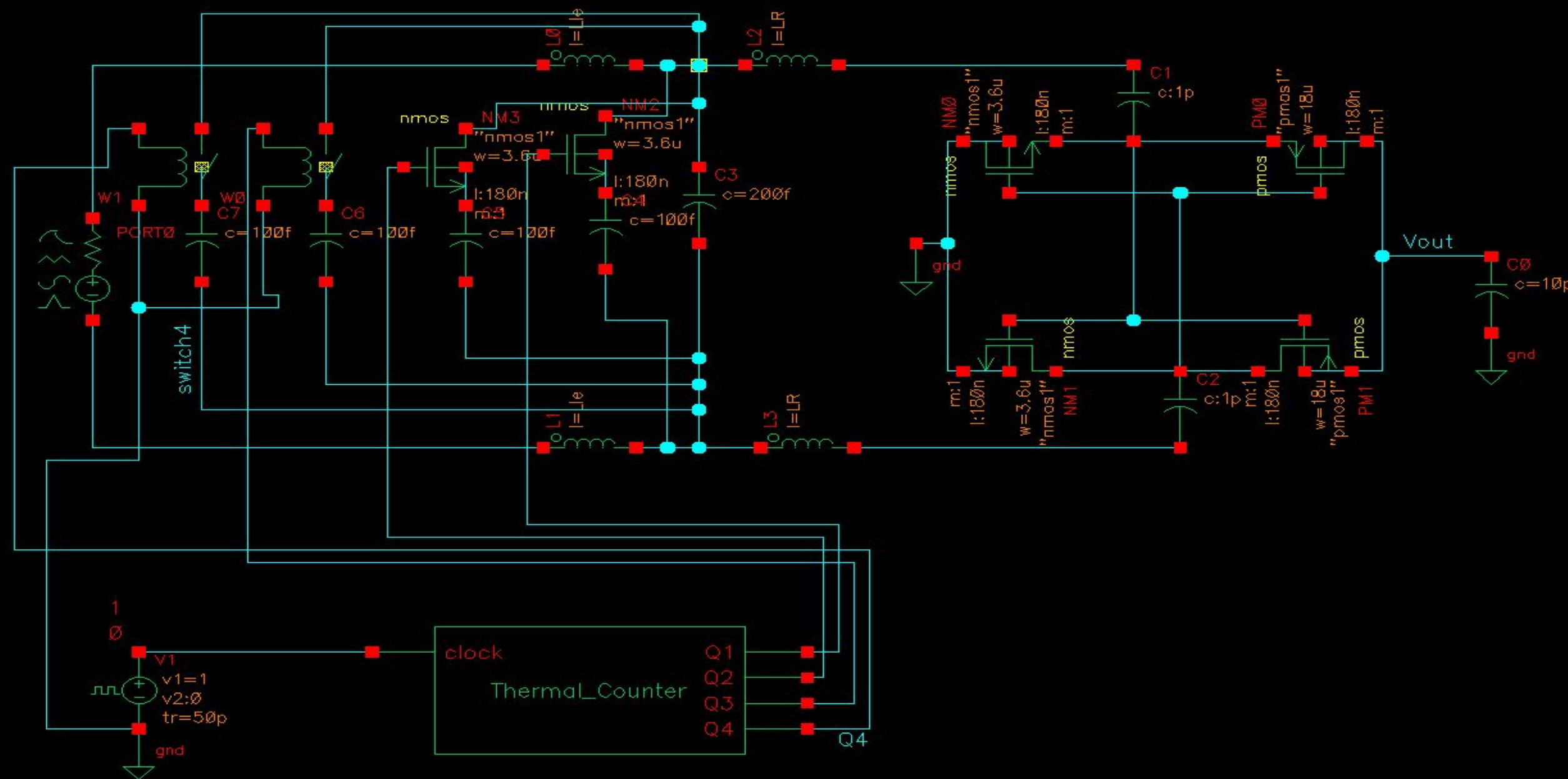

 


# RECONFIGURABLE CIRCUIT FOR RECTIFIER STAGES


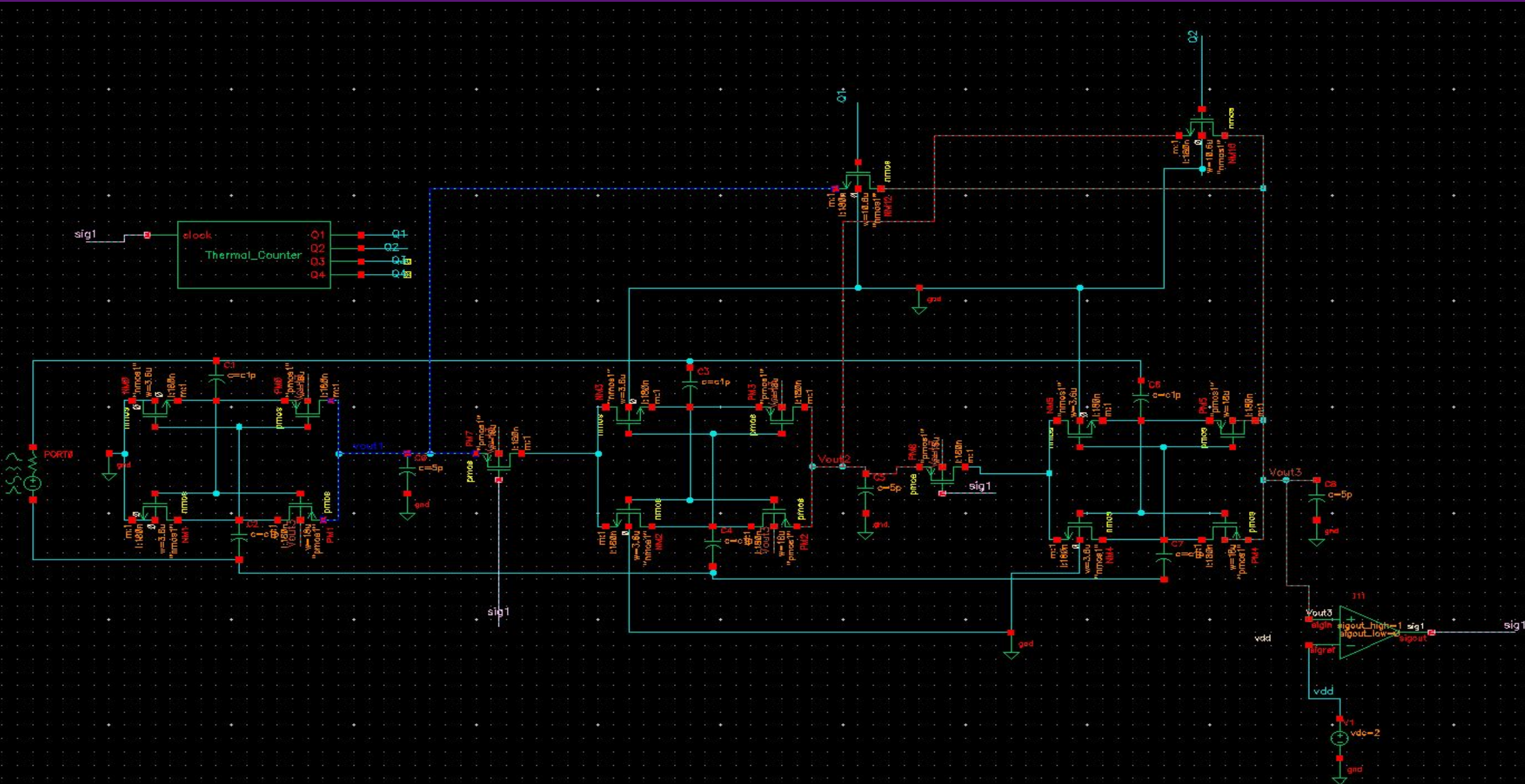
# MOTIVATION

- As input power varies from  $0_{\text{db}}$  to  $-30_{\text{db}}$ , we need multiple stages of rectifiers.
- A circuit for maintaining required number of stages for input power required and that can be achieved from this Reconfigurable Rectifier stage circuit.
- The Desired output from rectifier circuit can be controlled by the comparing voltage at Comparator.
- Circuits like LDO and buck convertor will have a loss in efficiency if their input is differ in large amount then desired output.



Edit Object Properties (on mayur.phd)

Apply To

only current

instance

Show

system

user

CDF

Browse

Reset Instance Labels Display

Property	Value	Display
Library Name	analogLib	off
Cell Name	vdc	off
View Name	symbol	off
Instance Name	V1	off

Add

Delete

Modify

User Property	Master Value	Local Value	Display
IvIgnore	TRUE		off

CDF Parameter	Value	Display
Noise file name		off
Number of noise/freq pairs	0	off
D C voltage	1.4 V	off
AC magnitude		off
AC phase		off
XF magnitude		off
PAC magnitude		off
PAC phase		off
Temperature coefficient 1		off
Temperature coefficient 2		off
Nominal temperature		off

OK

Cancel

Apply


Defaults

Previous

Next

Help

 A DESIRED 1.4 V FOR LDO CIRCUIT  
COMPARATOR WAS GIVEN 1.4 V



**Edit Object Properties (on mayur.phd)**

Apply To:

Show: ☐ system ☒ user ☒ CDF


Property	Value	Display
Library Name	analogLib	off
Cell Name	vdc	off
View Name	symbol	off
Instance Name	V1	off

User Property	Master Value	Local Value	Display
Ivsignore	TRUE		off

CDF Parameter	Value	Display
Noise file name		off
Number of noise/freq pairs	0	off
DC voltage	2 V	off
AC magnitude		off
AC phase		off
XF magnitude		off
PAC magnitude		off
PAC phase		off
Temperature coefficient 1		off
Temperature coefficient 2		off
Nominal temperature		off

## 2V OUTPUT SPECIFICATIONS



 

# LEARNINGS:

- IM NETWORKS
- Circuit Designing for D flip flops and basic gates with 180nm cmos technology.
- Circuit Designing for binary and thermal counters
- Reconfiguration circuits.
- Basic coding in verilog language.
- Introduced to cadence Tool
- Enjoyed the working experience for a real time Problem.

# Future plans:

- Increasing efficiency of reconfiguring rectifier stage circuit.
- 4 to 16 decoder for LDO circuit.
- Improvement of Impedance matching Network.
- Exploring Deep in RF circuit elements and improving efficiency for constraints.
- To check the overall Performance by connecting LDO to reconfigurable circuit and increase the efficiency



# REFERENCES:

- Efficient Dual Band RF Energy Harvesting Front End for Ultra Low Power Sensitive Passive Wearable Devices ,978-1-4799-6965-4/14 \$31.00 © 2014 IEEE DOI 10.1109/ISED.2014.25(paper).
- <https://ieeexplore.ieee.org/document/8067367>
- <https://ieeexplore.ieee.org/abstract/document/794456>

# THANK YOU